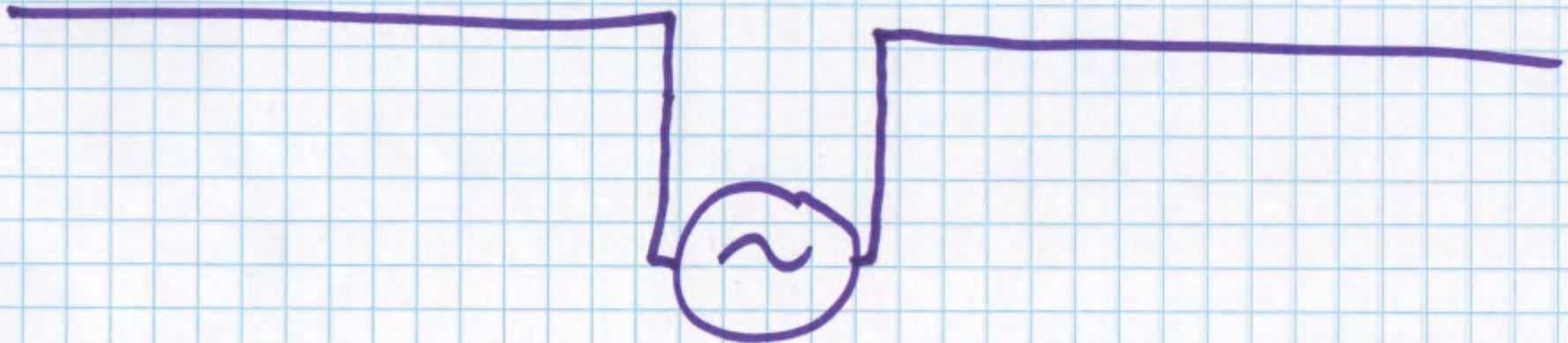


Transmission Lines

Chris Hamilton AESIT

2020 Jan 25


What are transmission
lines?




Co-axial



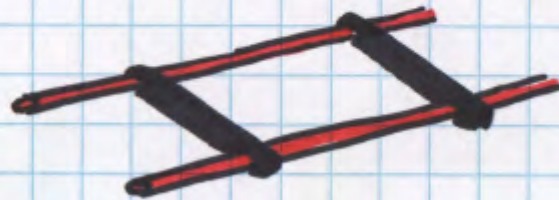Twin-lead
window-line,
ladder-line,
home brew





Wave guide

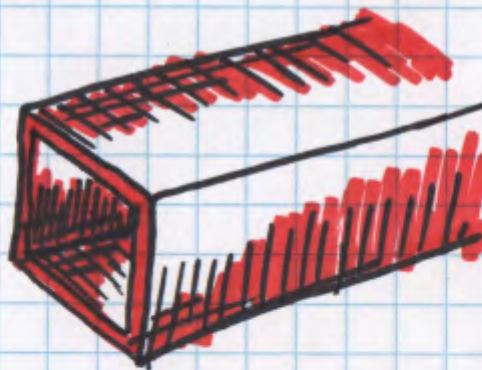


Stripline

Micro-stripline

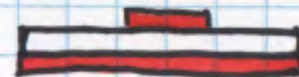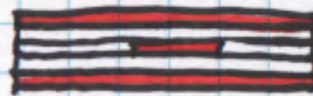

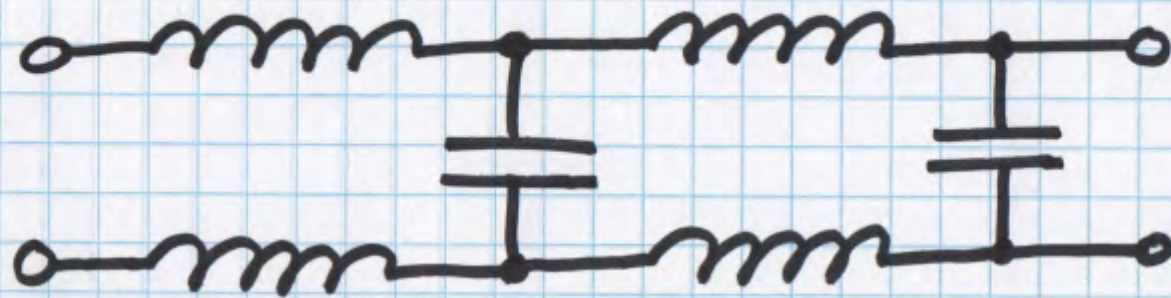Transmission lines behave
electrically like series
inductors & parallel capacitors



Keep this in mind!

It helps us understand things
later



Properties of transmission lines

Resistance & ohmic loss
conductors + dielectric

Characteristic Impedance

} Both
Measured
in Ohms
 Ω

Propagation velocity


Non-radiating

Frequency dependency

Characteristic Impedance


Regardless of load

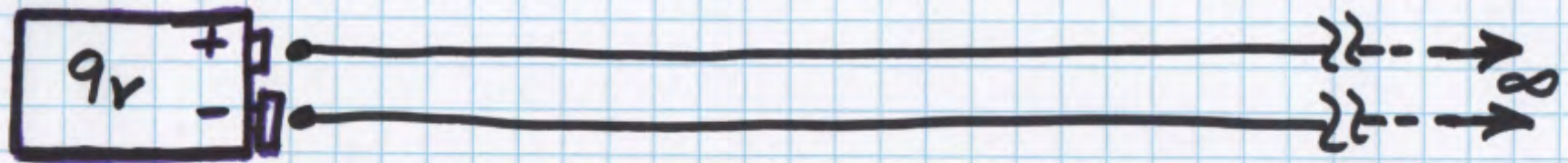What current flows
through the line when
a voltage is applied?



Water Analogy

(There's always a water analogy)

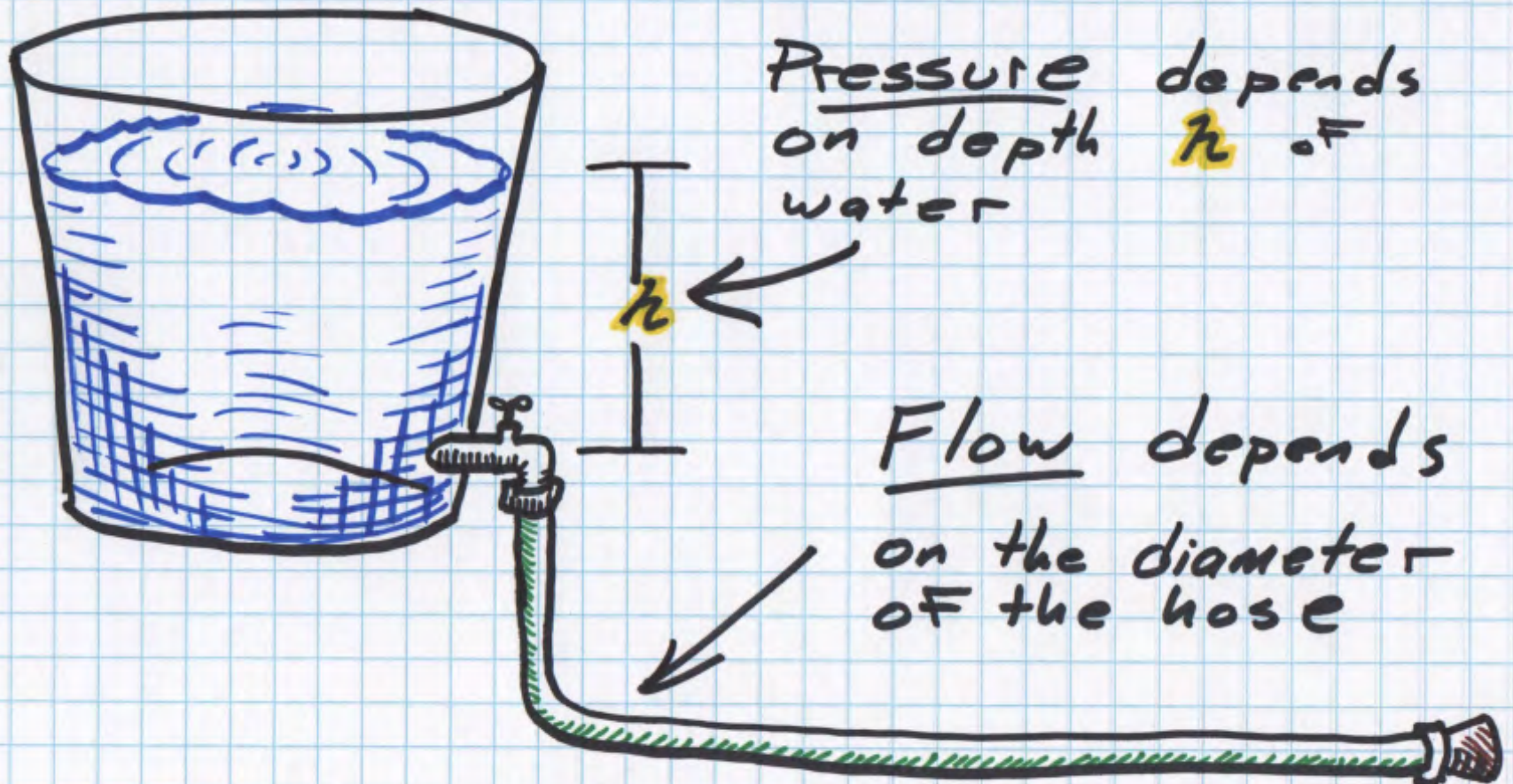

Voltage is like Pressure

Current is like Flow

$$\frac{\text{Voltage}}{\text{Current}} \quad \frac{\text{Pressure}}{\text{Flow}}$$

These ratios are
a property of the
line - which depend
on its physical construction

$$\frac{\text{Voltage}}{\text{Current}} = \frac{E}{I}$$

$$E = I \cdot R$$

$$\frac{E}{I} = R$$


$$R = \frac{E}{I}$$

300 Ω
line

9V
battery

$$300 = \frac{9}{I}$$



$$I = \frac{9}{300} = 0.03 \text{ A}$$

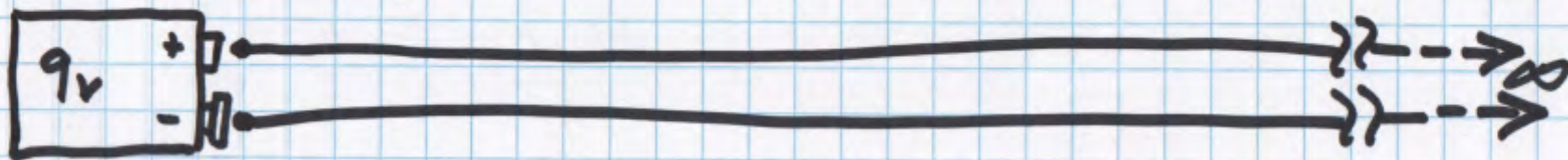


What determines char. Imp.?

- Distance between conductors
- Permittivity of insulation between conductors (Dielectric constant)
- Size of conductors
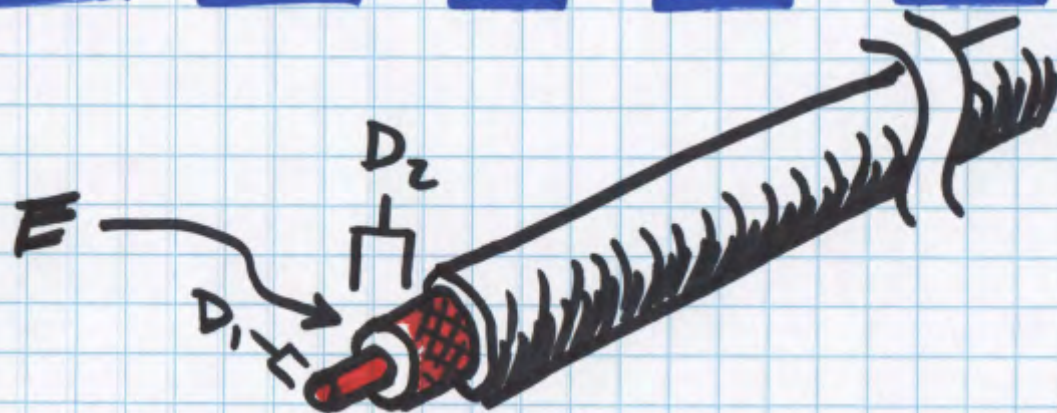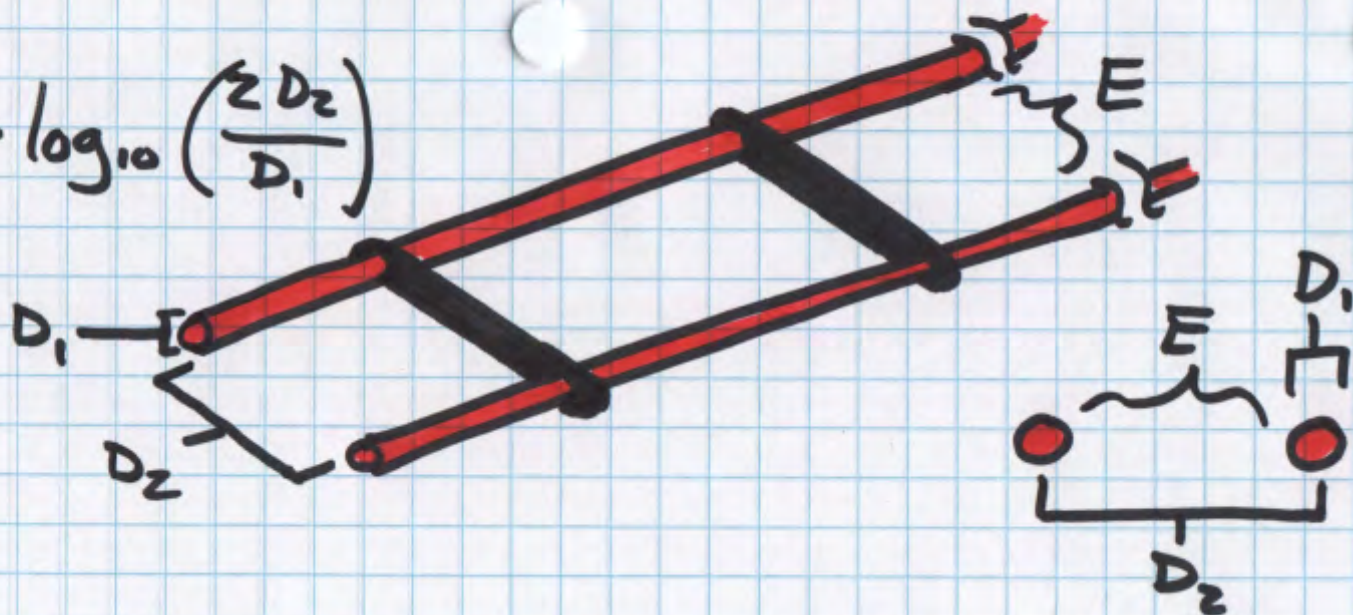
$$Z_0 = \frac{276}{\sqrt{E}} \cdot \log_{10} \left(\frac{2D_2}{D_1} \right)$$



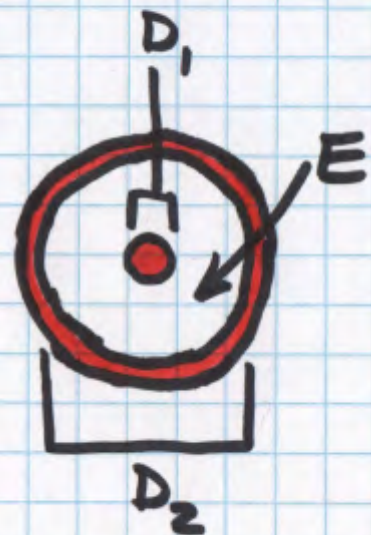
$$Z_0 = \frac{138}{\sqrt{E}} \cdot \log_{10} \left(\frac{D_2}{D_1} \right)$$




Line Loss

Transmission lines are made
from real-world materials



idealized
model

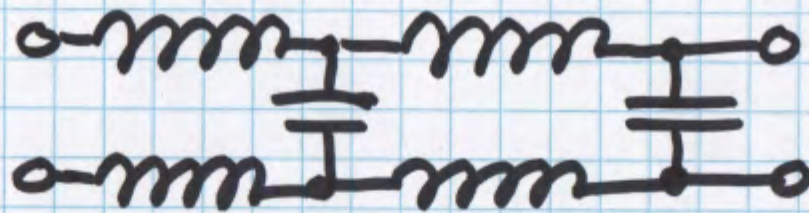

more
realistic

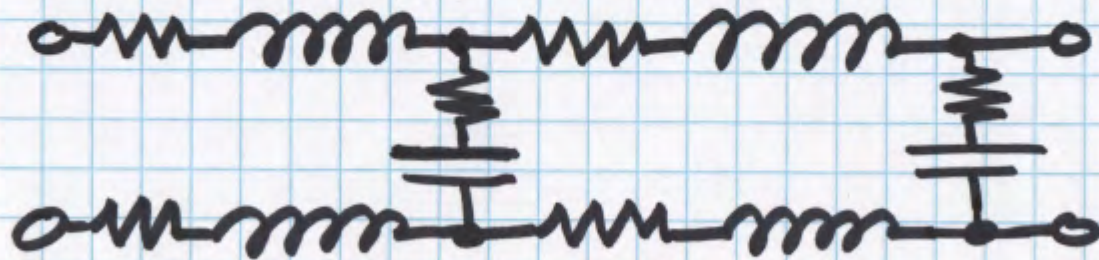

Propagation Velocity / Velocity Factor

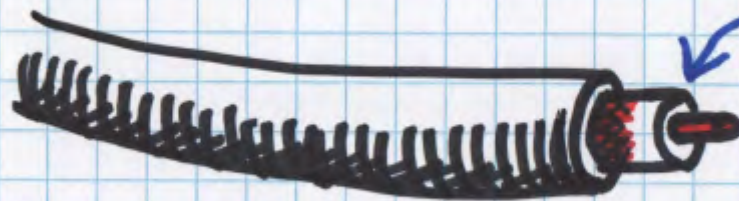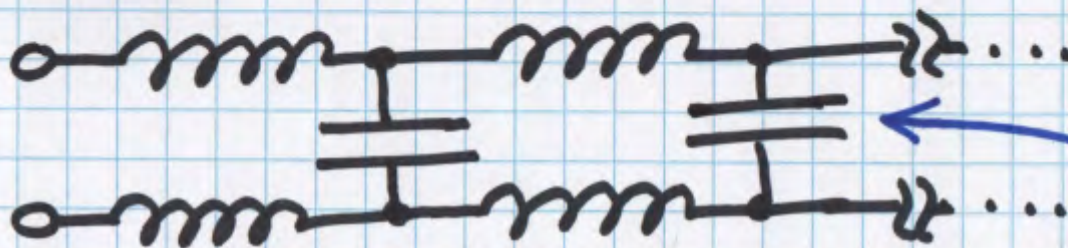

some
insulator

E : dielectric constant
of insulation

$$VF = \frac{1}{\sqrt{E}}$$

VACUUM
 $E = 1$

$$VF = \frac{1}{\sqrt{1}} = 1$$

AIR
 $E = 1.00054$

$$VF = \frac{1}{\sqrt{1.00054}} \approx \frac{1}{1} \approx 1$$

POLYETHYLENE
 $E = 2.26$

$$VF = \frac{1}{\sqrt{2.26}} \approx \frac{1}{1.5} \approx \frac{2}{3}$$

Frequency Dependency

Loss : Capacitor ESR varies

Dialectric losses


Leaky shielding

Construction imperfections


skin depth

Distance b/w conductors

Loads & Matching



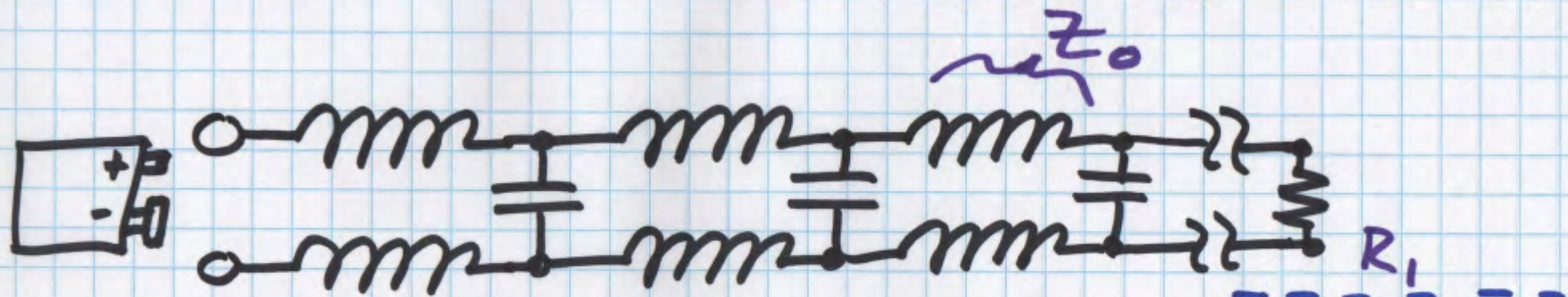


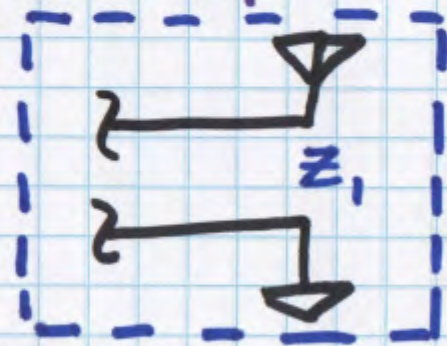If $R_L = Z_0$ then the
Signal source thinks
the line is infinitely long




matched
condition

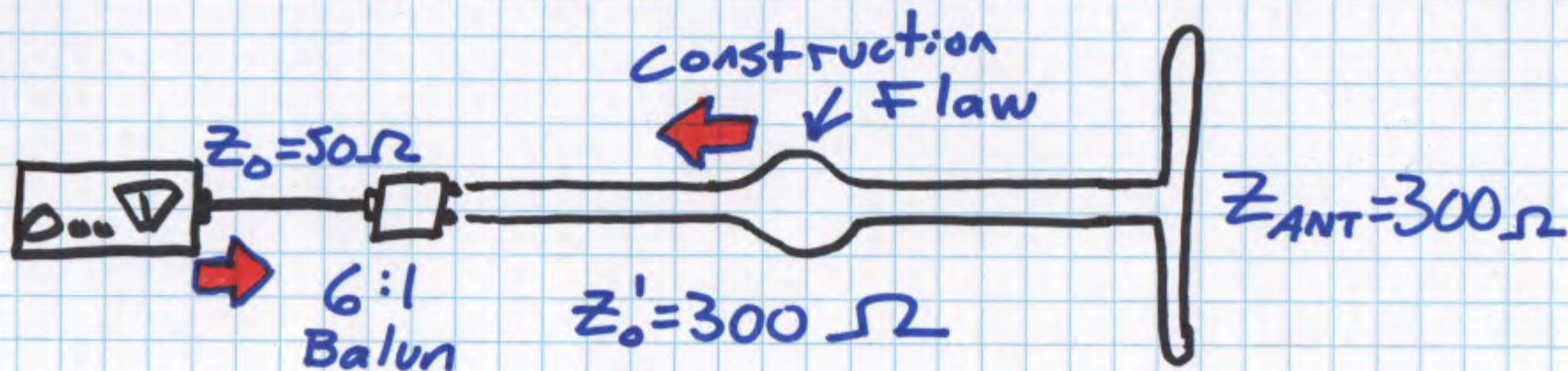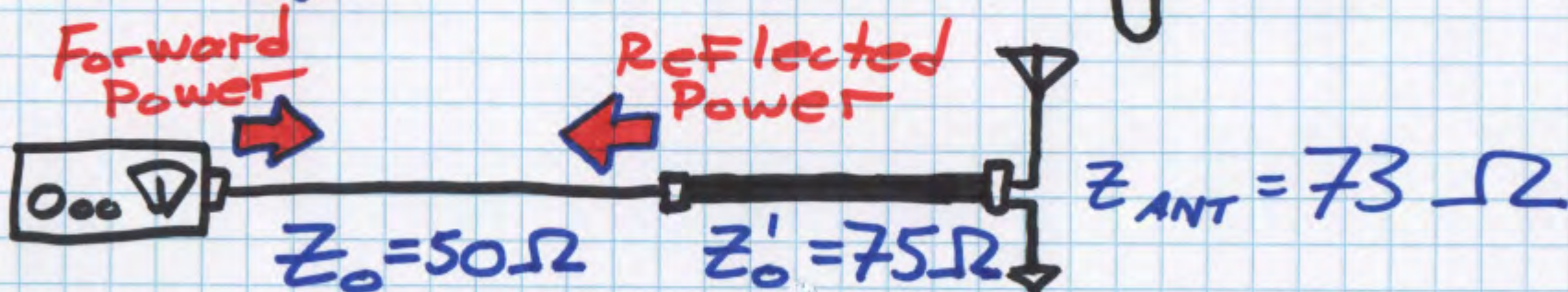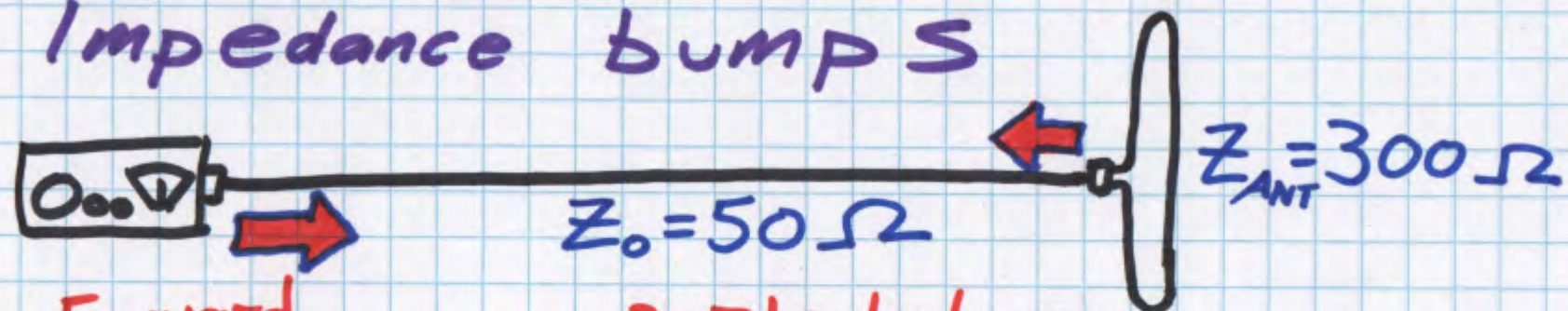
Un-matched Loads, Discontinuity, and Impedance bumps




There's Always a Water Analogy

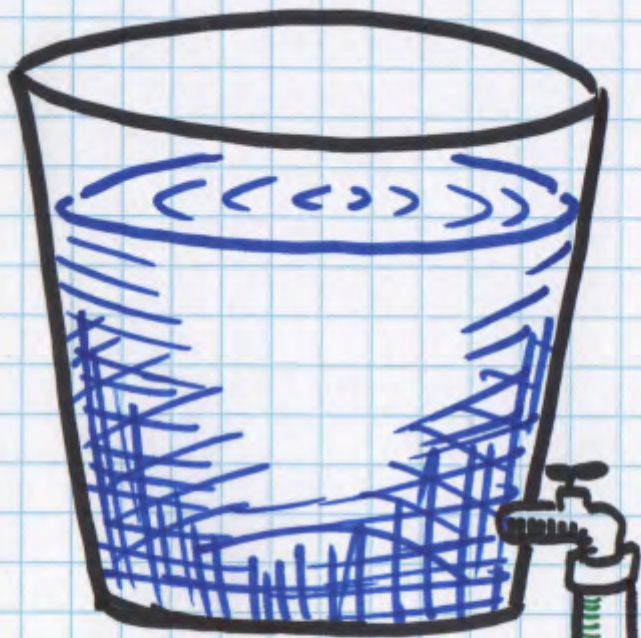

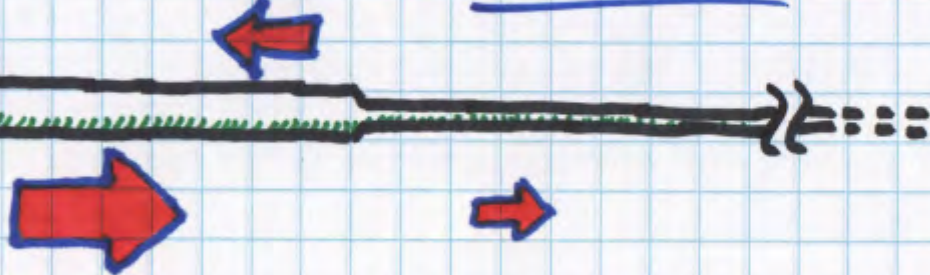
Flow is interrupted
at discontinuity
some power rebounds
i.e. reFlected




Reflection

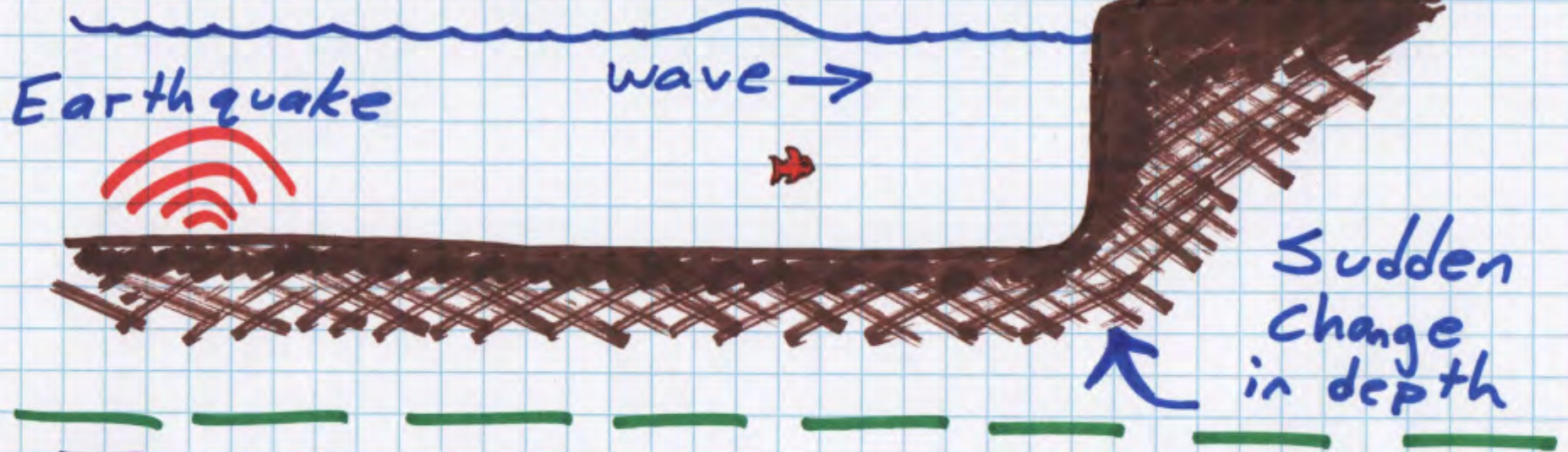

Transformation

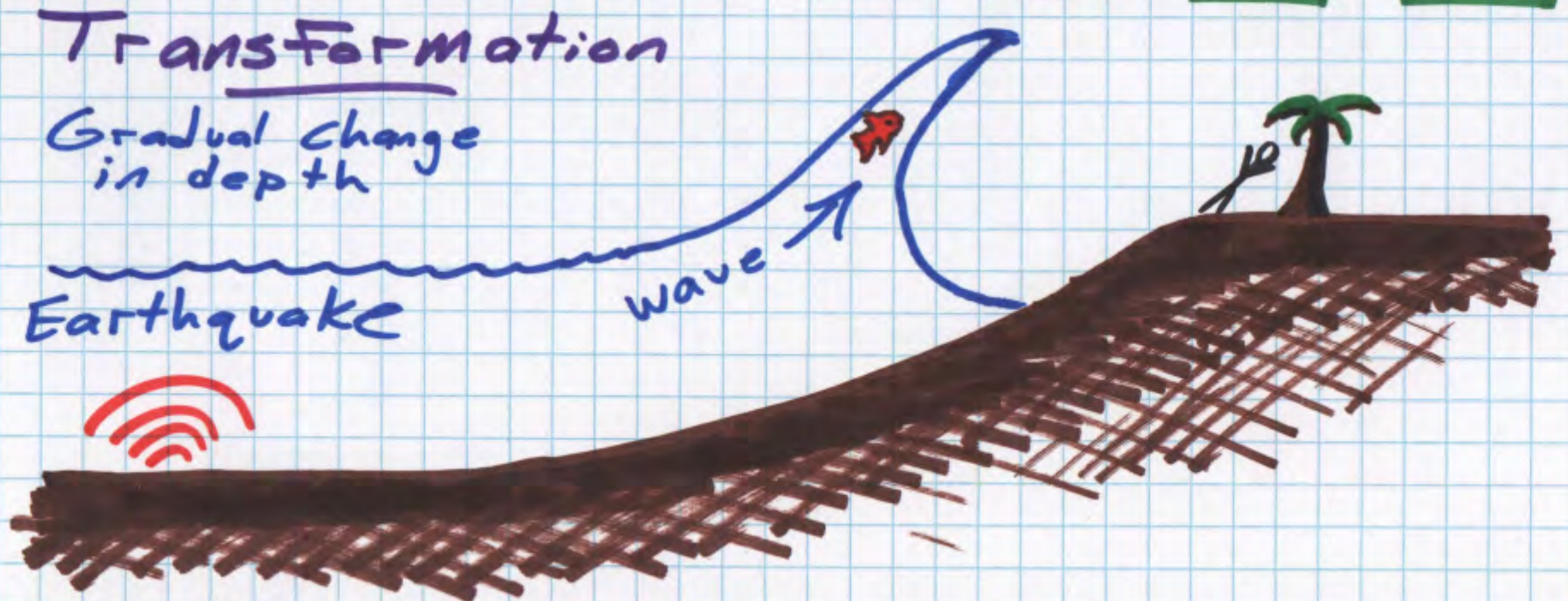

Reflections cause power loss

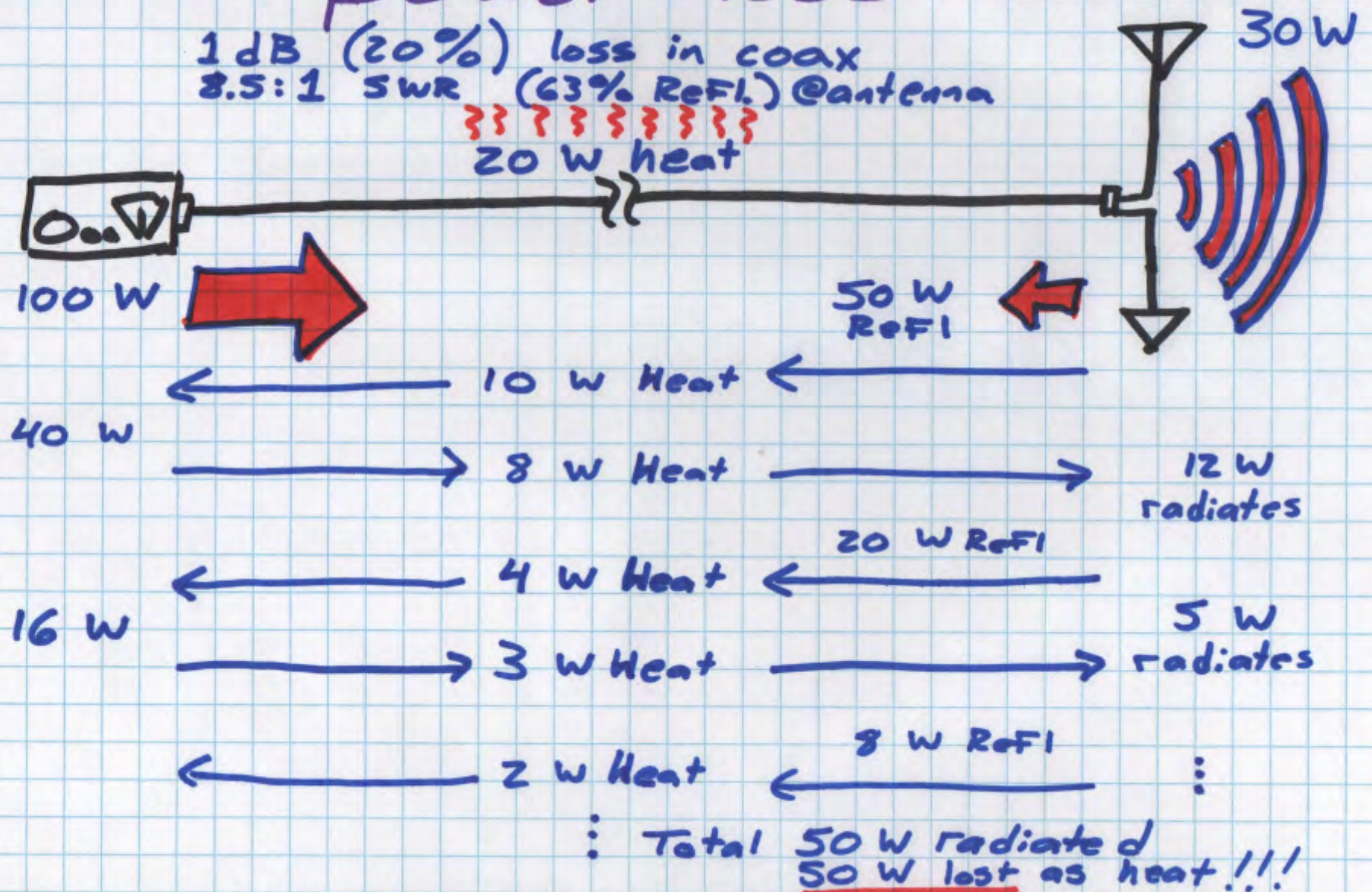

Reflections Cause power loss

- Due to power traversing lossy transmission line multiple times
- Lower loss line = better performance

Hardline, Helix, Ladder Line

$$100 \text{ W} \cdot 1 \text{ dB line loss} \cdot 8.5:1 \text{ SWR} = 50\% \text{ loss} \quad (((50 \text{ W})))$$



$$100 \text{ W} \cdot 0.054 \text{ dB line loss} \cdot 8.5:1 \text{ SWR} = 6\% \text{ loss} \quad (((94 \text{ W})))$$

"Loss due to SWR"

Forward Wave



Reverse Wave

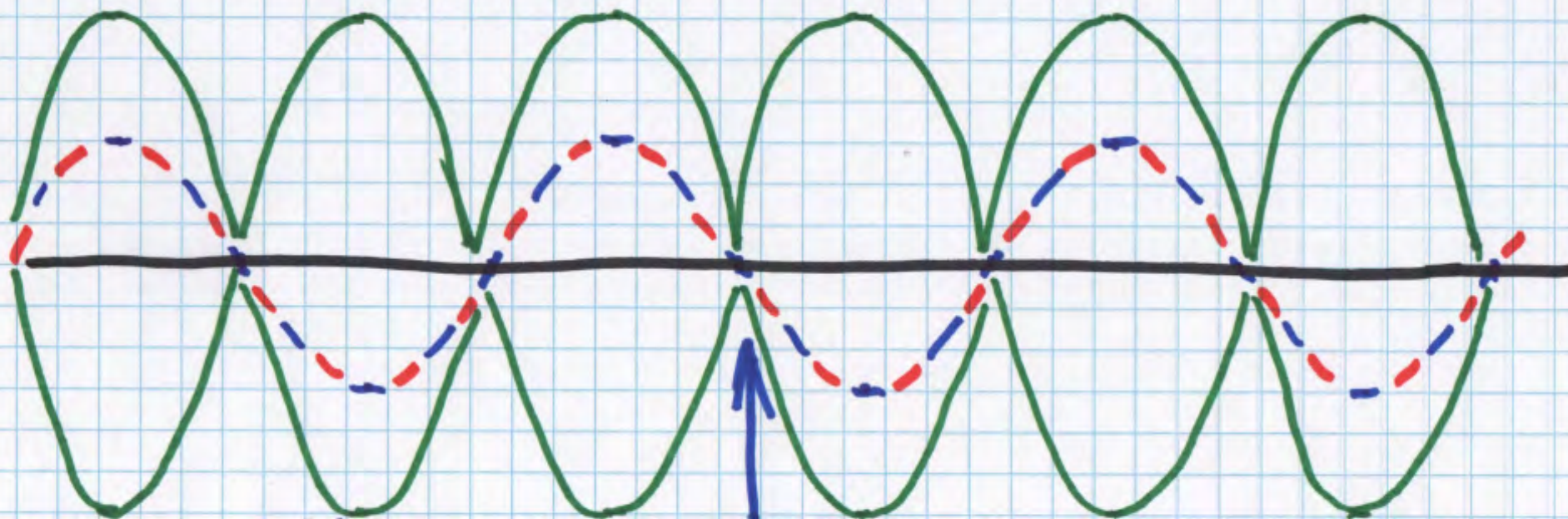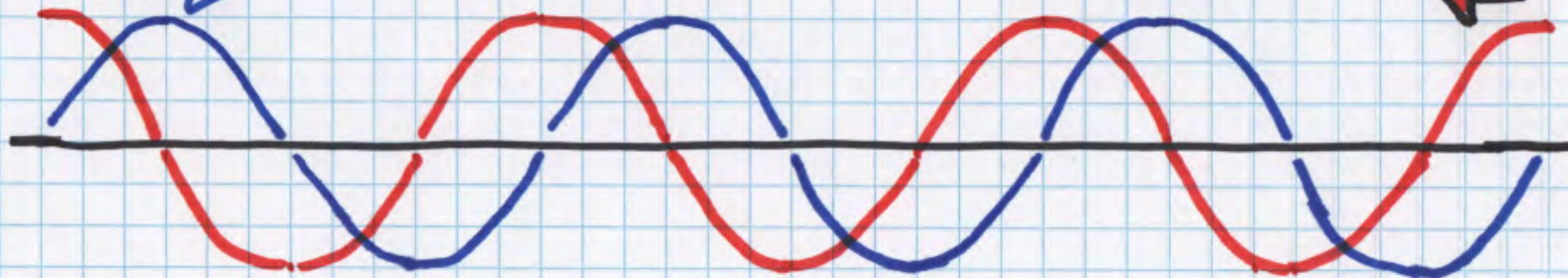

$$SWR = \frac{V_{max}}{V_{min}}$$

V_{min}

V_{max}

SWR Lessons

With short runs of
low-loss line SWR
is not a big deal

-UNLESS-

- Voltages get high enough
to Flash over
- Currents get high enough
to start a Fire


Useful
~~Stupid~~


Transmission Line
Tricks

Phasing Lines

We are working with wavelengths
From $\frac{3}{4}$ to a few dozen meters.

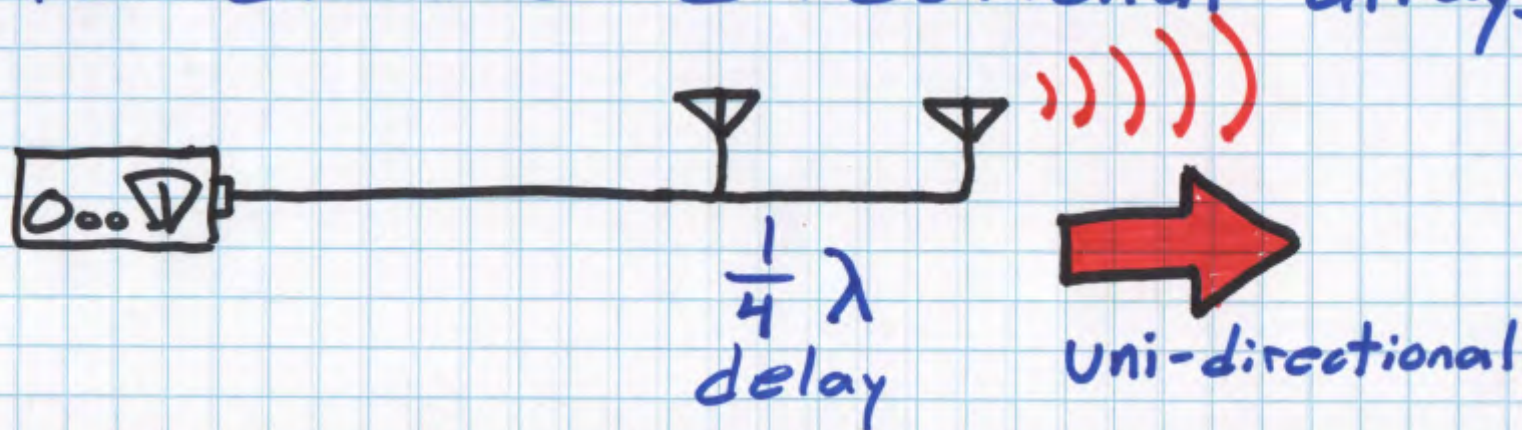
Use delay lines to deliver
signals slightly out of phase
to create directional arrays



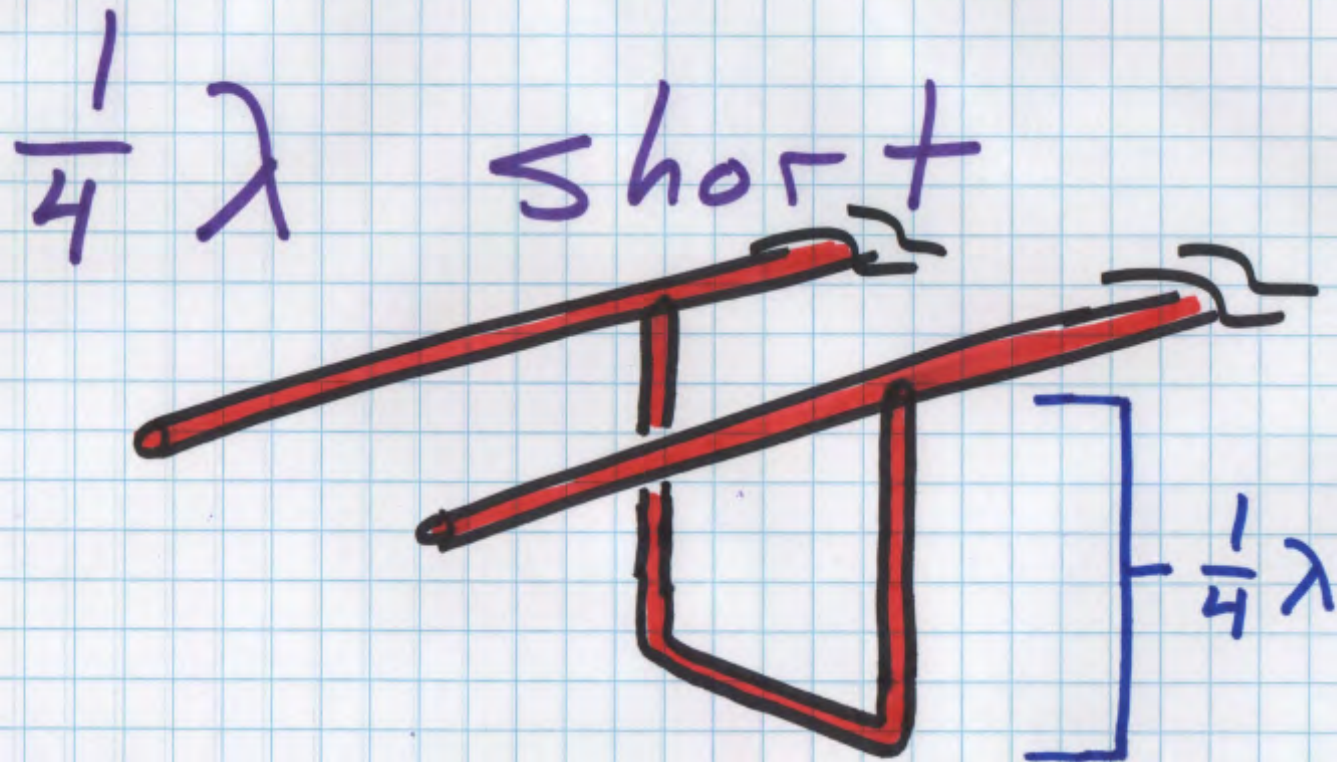


- Provides DC ground
- Invisible to RF
- Narrow-band (very)

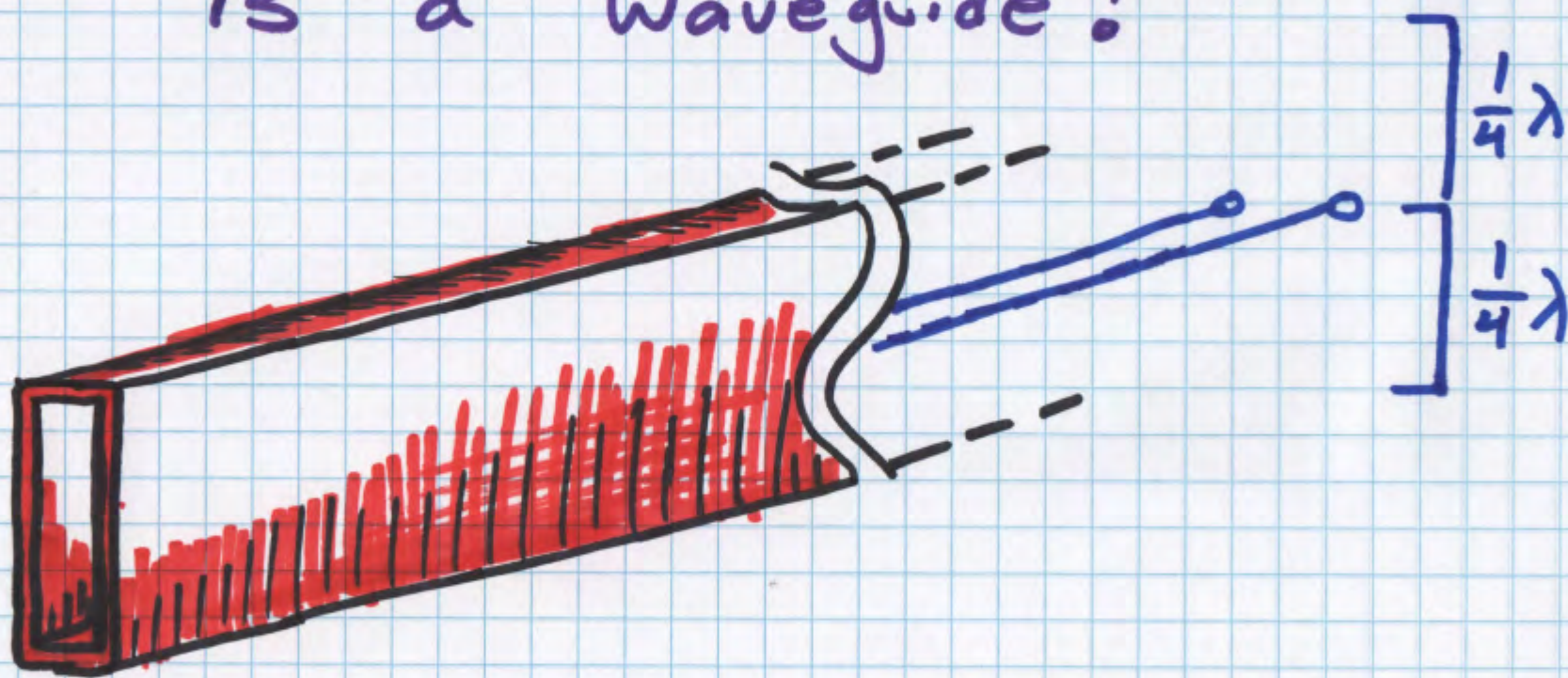
Continuous $\frac{1}{4} \lambda$ short
Is a Waveguide!



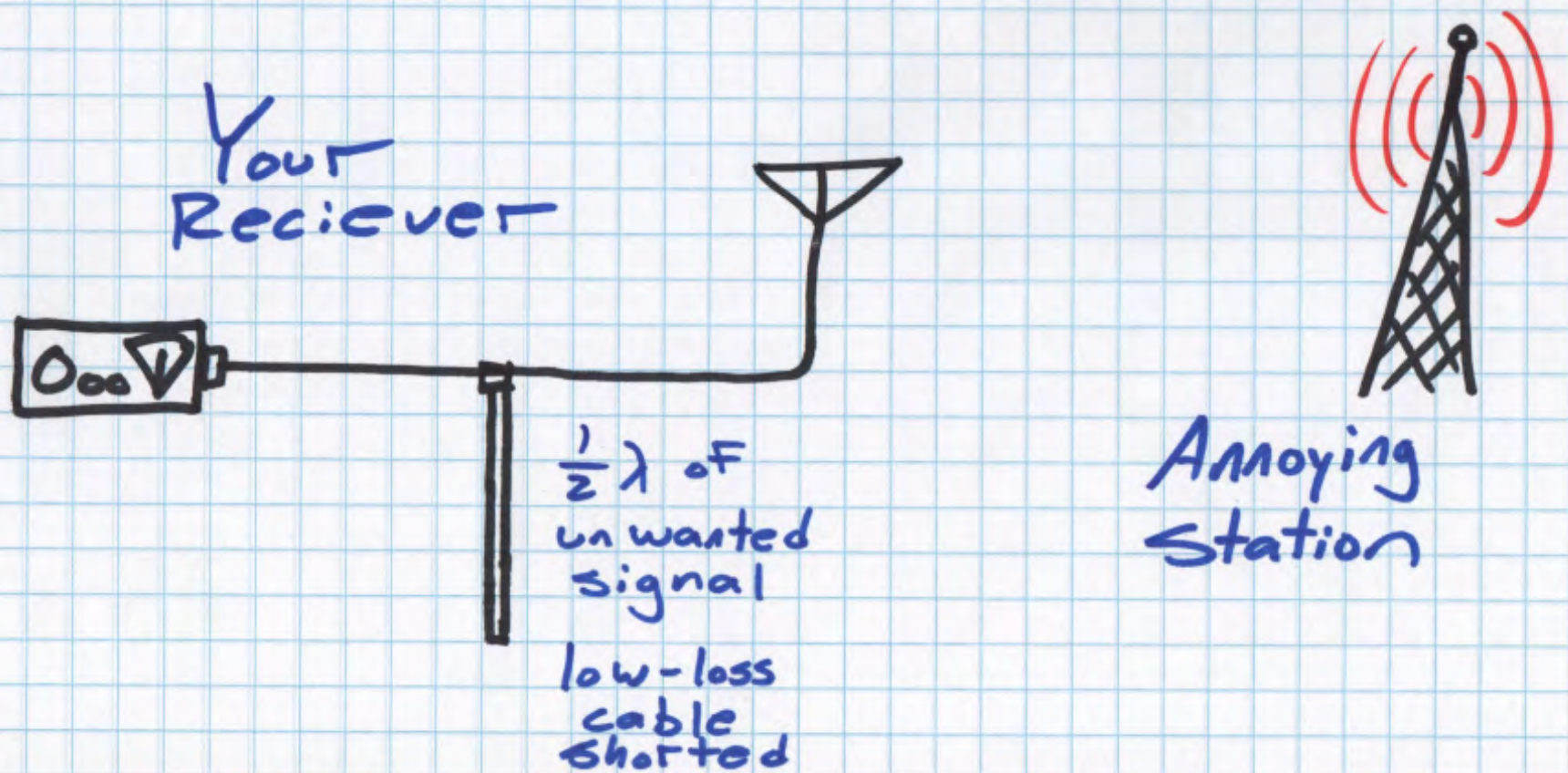$\frac{1}{2} \lambda$ Short is
a narrow-band notch filter



Impedance Transformer

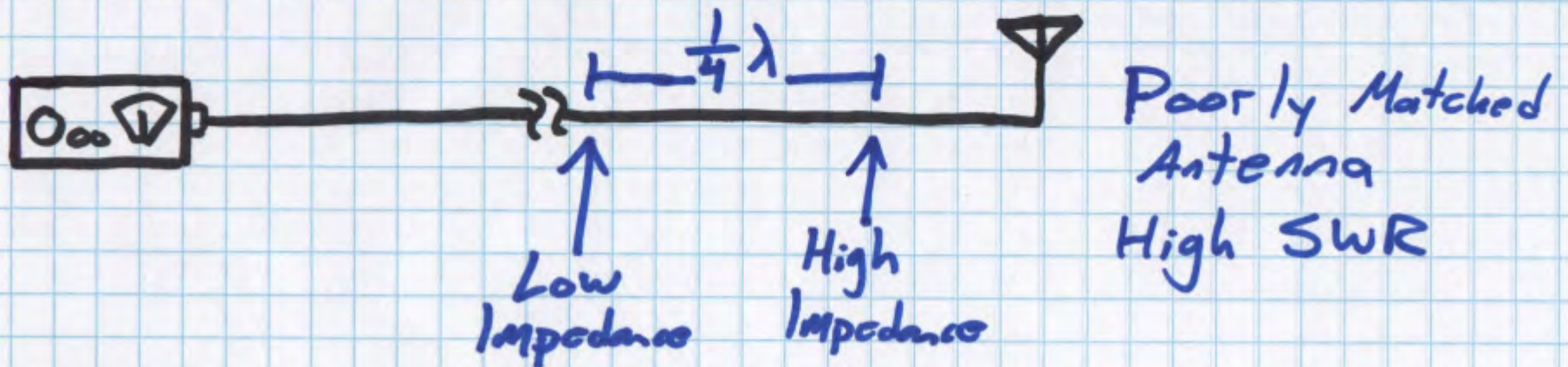


Maybe you can shorten
or lengthen your transmission
line to find a reasonable
match to your transmitter.

Hint: G5RV does exactly this!

Impedance Transformer

Coax Loop 4:1 Balun

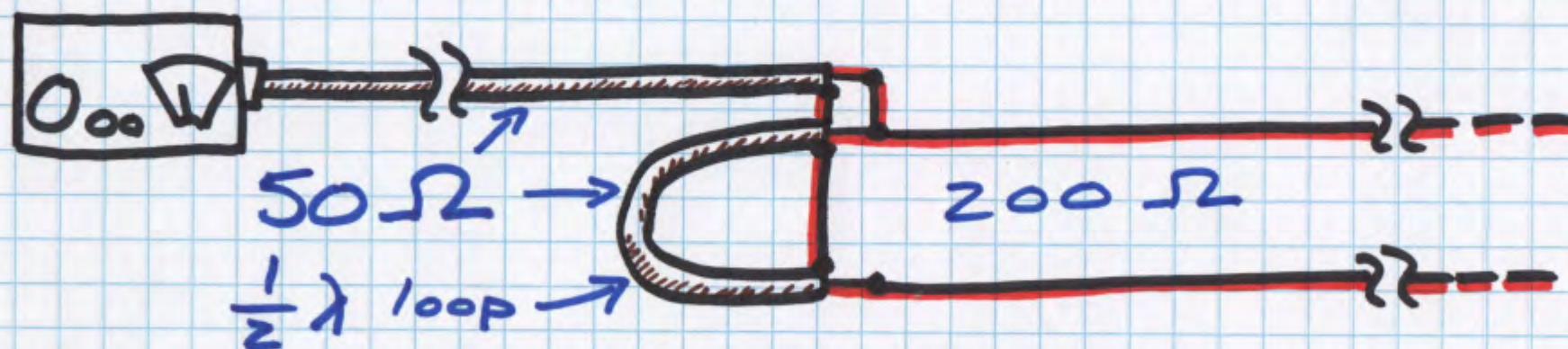

- Connect all shields
- Connect input center to one side of loop center
- Loop centers are 200 Ω output

Further resources

- Basic Antennas; Joel Hallas W1ZR
- Standing up for Standing Waves; Bill Hays
- Similarities in Wave Behavior; Dr JN Shive, AT&T Archives (YouTube)